 


## Work for Digital Electronics Supervision IV


Please attempt all the core items as usual and send your work to me by 1800 on Friday, 7th November. All your answers, working and any additional thoughts should be written up in L<sup>A</sup>T<sub>E</sub>X and emailed to [mti20@cam.ac.uk](mailto:mti20@cam.ac.uk).

### Core questions

1. Examples sheet exercises 19–22.
2. For what values of  $R_a$ ,  $R_b$  and  $R_c$  is the resistor network on the left of the following diagram equivalent to the resistor network on the right?



 3. Find the capacitance across terminals  $A$  and  $B$  when the switch  $S$  is open, and when it is closed.



4. Examination question: 2012 Paper 2 Question 2 (attached towards the end of this document).
5. (a) Give a qualitative explanation of current flow across a *p-n junction* in a semiconductor diode.  
(b) Why is there a depletion layer in the immediate vicinity of the junction?  
(c) Why is a resistor usually placed in series with a light-emitting diode? Given an LED which is to be driven from a 5V supply, what should be the value of the series resistor?
6. (This question goes a little beyond the course, but you should be able to tackle it with the aid of Google if you're brave enough.)

Examination question: 2007 Paper 7 Question 11 (attached at the end of this document).


### Extension questions

7. (Omitted for 2014.)

COMPUTER SCIENCE TRIPOS Part IA – 2012 – Paper 2

2 Digital Electronics (IJW)

 - (a) With the aid of appropriate diagrams, show how the Source–Drain current that flows in a p-channel MOSFET is controlled by the applied Gate–Source voltage. [4 marks]
- (b) (i) Draw the circuit diagram of a NOT gate that comprises an n-channel MOSFET and a resistor  $R$ . [2 marks]
- (ii) For the NOT gate in (b)(i), plot the relationship between the input voltage,  $V_{in}$  and the output voltage,  $V_{out}$ . Assume that the power supply voltage  $V_{DD} = 12\text{ V}$ ,  $R = 1\text{ k}\Omega$ , and that the MOSFET has the characteristics given in the following figure. [4 marks]



- (c) For the NOT gate in (b), calculate the power dissipated by the entire gate and that by resistor  $R$  alone, when  $V_{in} = 12\text{ V}$ . [4 marks]
- (d) The stray capacitance present at the output of the NOT gate in (b) can be represented by a capacitor,  $C = 100\text{ nF}$  connected between the gate output and  $0\text{ V}$ . Also assume that the MOSFET has an ON resistance  $R_{on} = 100\ \Omega$ . The input signal,  $V_{in}$ , is a  $1\text{ kHz}$  square wave with minimum and maximum amplitudes of  $0\text{ V}$  and  $12\text{ V}$  respectively.
- (i) Sketch the output signal waveform,  $V_{out}$ , of the NOT gate being sure to include indicative rise and fall times and voltage levels. [4 marks]
- (ii) How could the rise-time of  $V_{out}$  be reduced and what would be the impact of your proposed solution on the power dissipation of the circuit?

## 2007 Paper 7 Question 11

### VLSI Design

- (a) Sketch a transistor-level circuit for a 2-input AND gate in static CMOS. [2 marks]
- (b) Consider the design of a 16-input AND gate in static CMOS.
- (i) Explain why the 2-input design could not simply be scaled up. [2 marks]
  - (ii) Sketch alternative designs using two and four levels of NAND and NOR gates. [2 × 2 marks]
  - (iii) Use logical effort to estimate the delay of both the designs, assuming that the conducting channel in a pFET has twice the resistance of that in an nFET. [10 marks]
  - (iv) Determine the approximate value of the electrical effort at which their speeds are equal. [2 marks]